
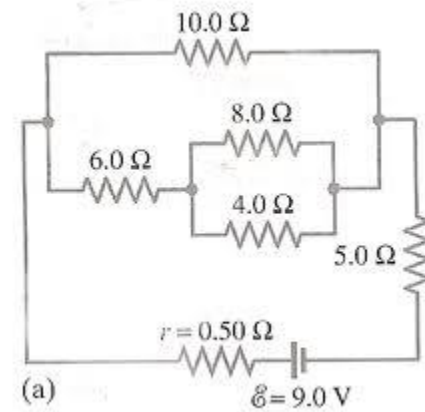


16.5


Parallel Circuits

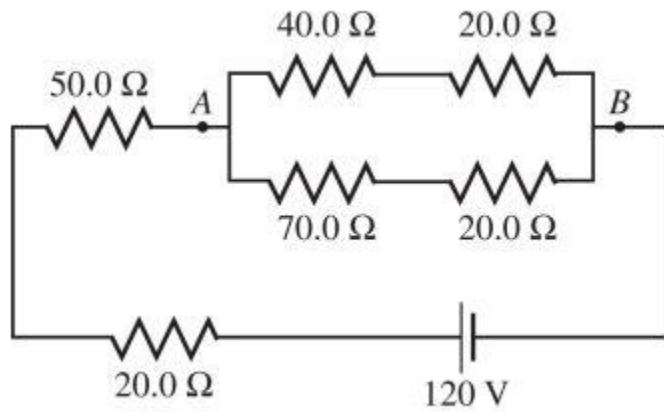

Parallel Circuits

In a **parallel circuit** having three lamps, each electric device has its own path from one terminal of the battery to the other.

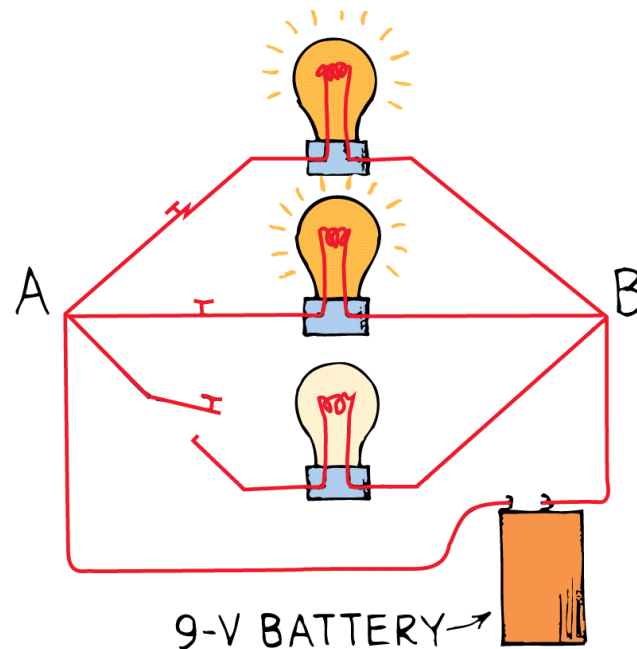
There are **separate pathways** for current, one through each lamp.



Parallel Circuits



In contrast to a series circuit, the parallel circuit is completed whether all, two, or only one lamp is lit.

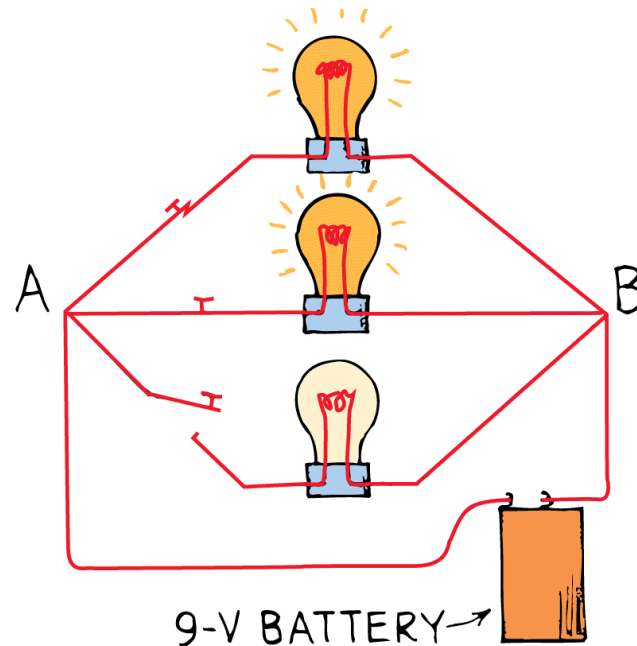A break in any one path does not interrupt the flow of charge in the other paths.



Parallel Circuits

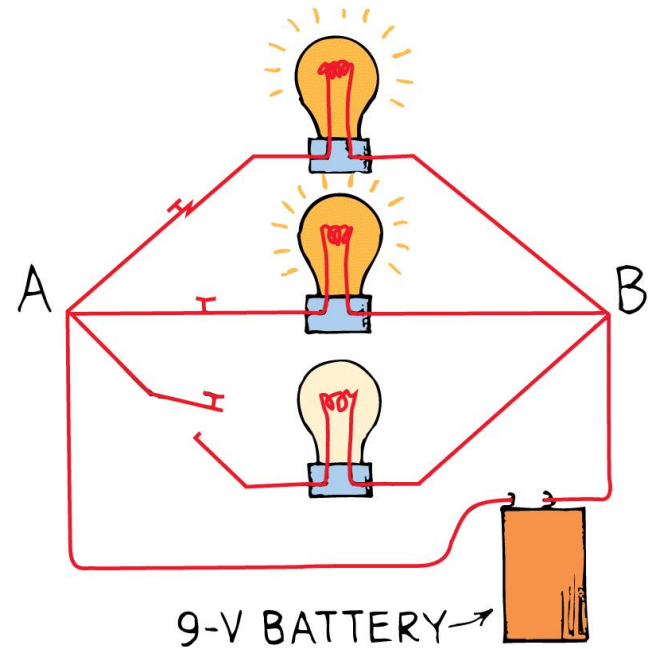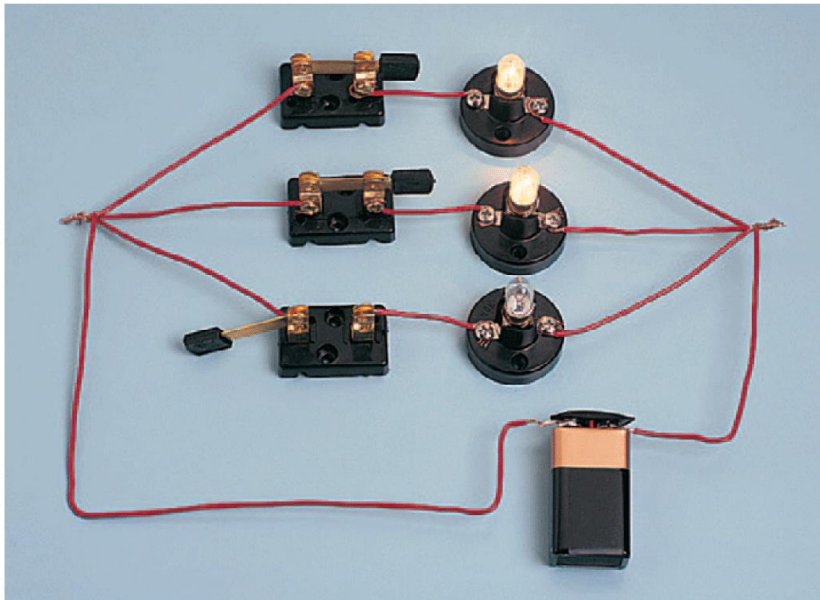In this parallel circuit, a 9-volt battery provides 9 volts across each activated lamp. (Note the open switch in the lower branch.)




Parallel Circuits

CONCEPT CHECK

What happens if one device in a parallel circuit fails?

A break in any one path does not interrupt the flow of current in the other paths.

Resistance in a Parallel Circuit

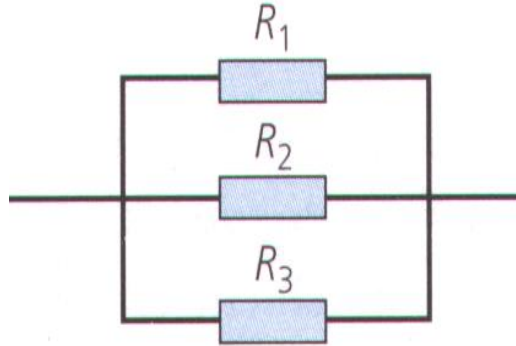


The reciprocal of the total resistance is equal to the sum of the reciprocals of individual resistance.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Resistance in a Parallel Circuit

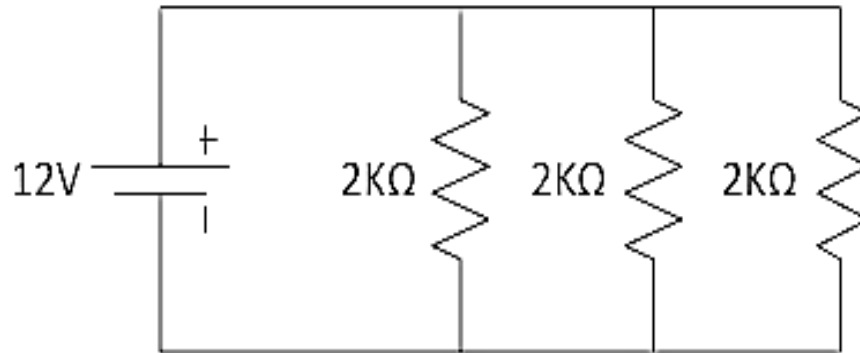Example #1


What is the equivalent resistance of the following circuit?



Resistance in a Parallel Circuit

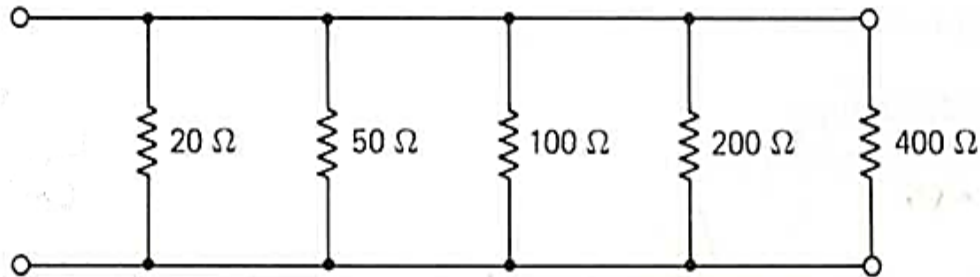Example #2:


What is the equivalent resistance of the following:



Voltage in a Parallel Circuit


Each device connects the same two points A and B of the circuit. The voltage is therefore the same across each device.

$$(V_T = V_1 = V_2 = V_3)$$

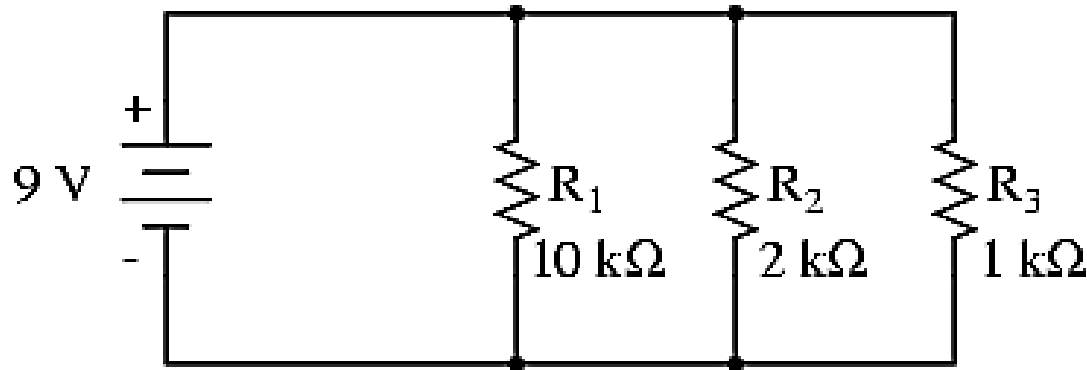


Current in a Parallel Circuit

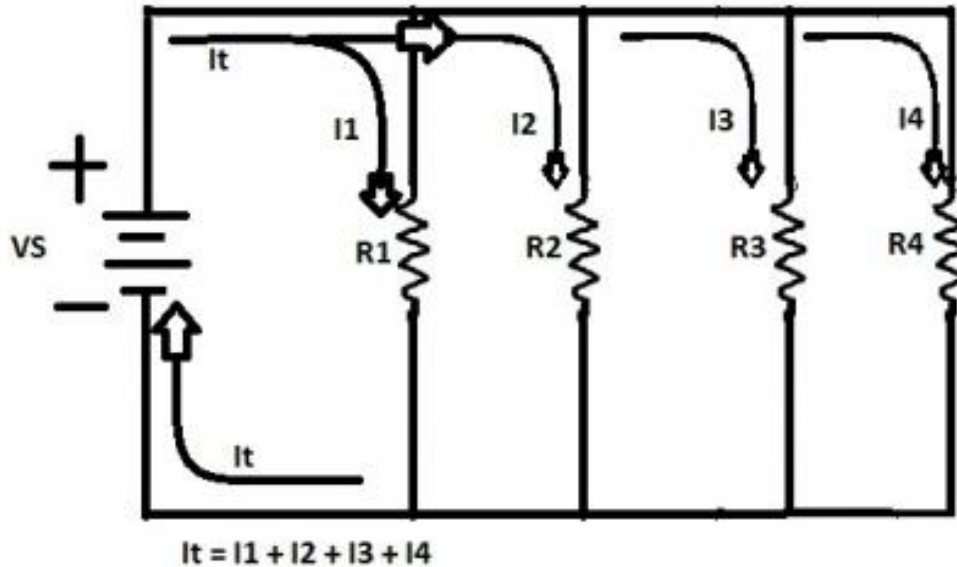- The total current divides among the parallel branches
- The total current is the sum of the currents in its branches.



Current in a Parallel Circuit

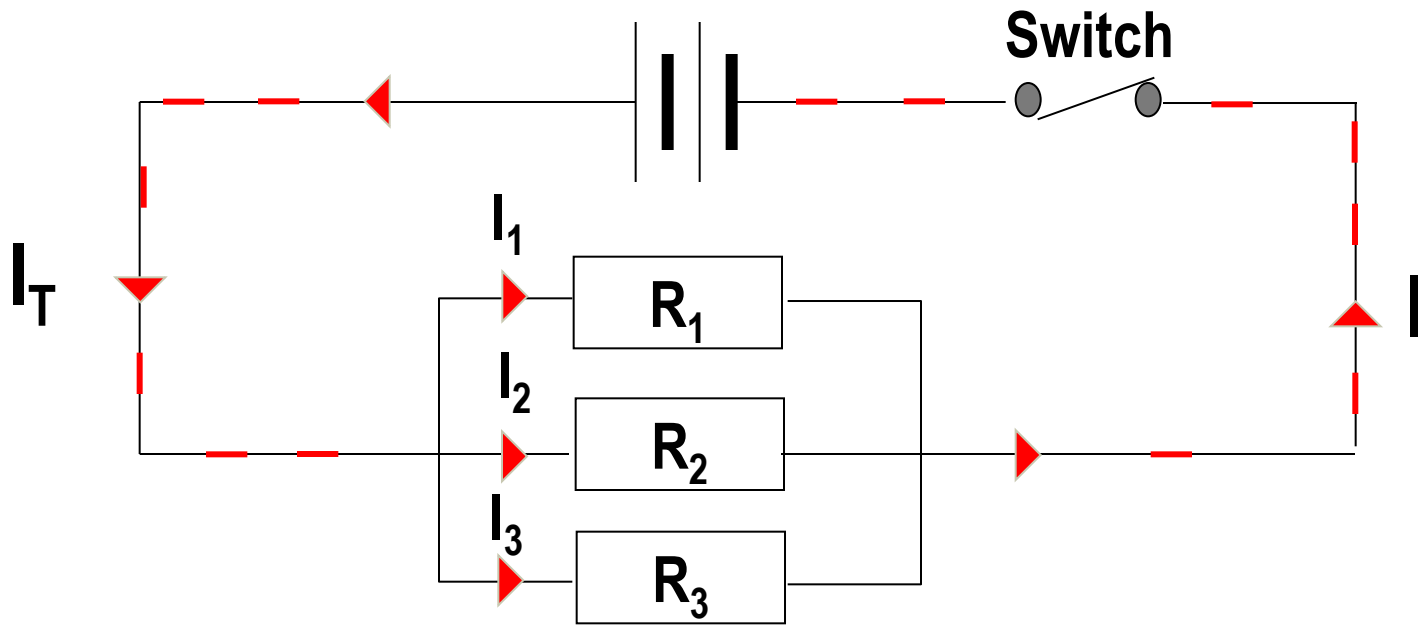

The main current is equal to the sum of the sub-currents

$$I_T = I_1 + I_2 + I_3$$

Parallel Circuits

CONCEPT CHECK


How are voltage, current and resistance calculated in a parallel circuit?

- *The voltage is the same across each device.*
- *The total current divides among the parallel branches.*
- *The total current is the sum of the currents in its branches.*
- *The reciprocal of the total resistance is equal to the sum of the reciprocals of individual resistance.*

Parallel Circuits Assessment Questions

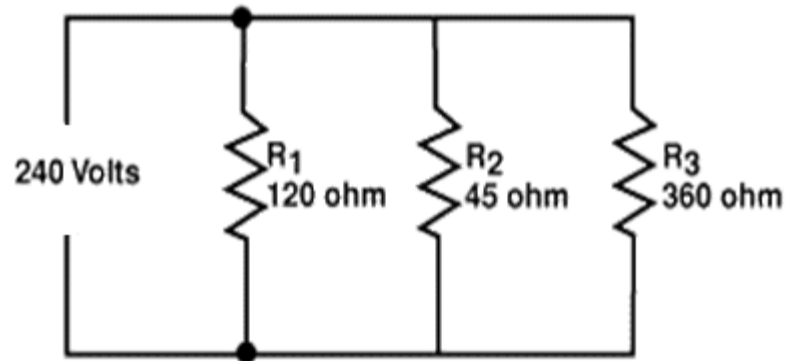
Example #3:

Use a VIRP table to calculate the values for the circuit below.



Parallel Circuits Assessment Questions

Example #3

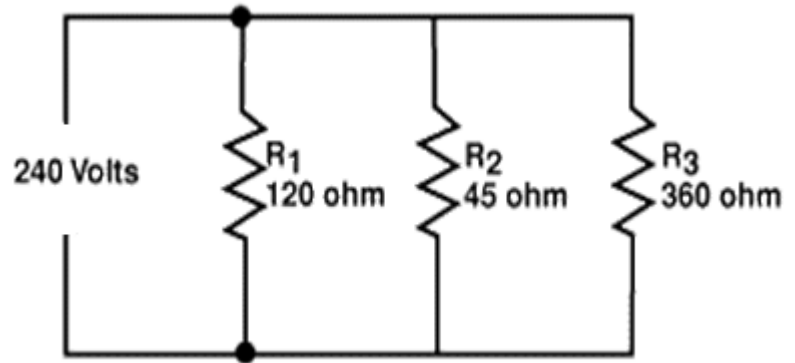


VIRP Table				
	V	I	R	P
R1				
R2				
R3				
Total				

Parallel Circuits Assessment Questions

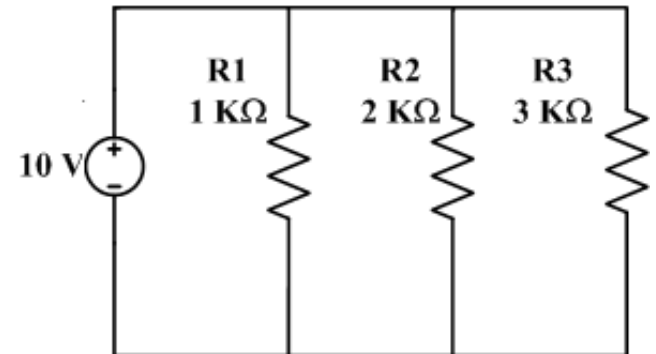Example #4:


A 10-volt supply is supplied to three resistors that are connected in parallel. Calculate:

- The combined resistance
- The total current flowing in circuit
- The current in the $2\text{-k}\Omega$ resistor
- The power in the $3\text{-k}\Omega$ resistor



Parallel Circuits Assessment Questions

Example #4:

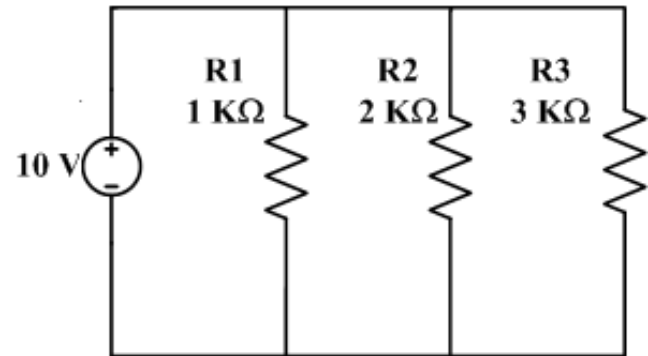

VIRP Table				
	V	I	R	P
R1				
R2				
R3				
Total				